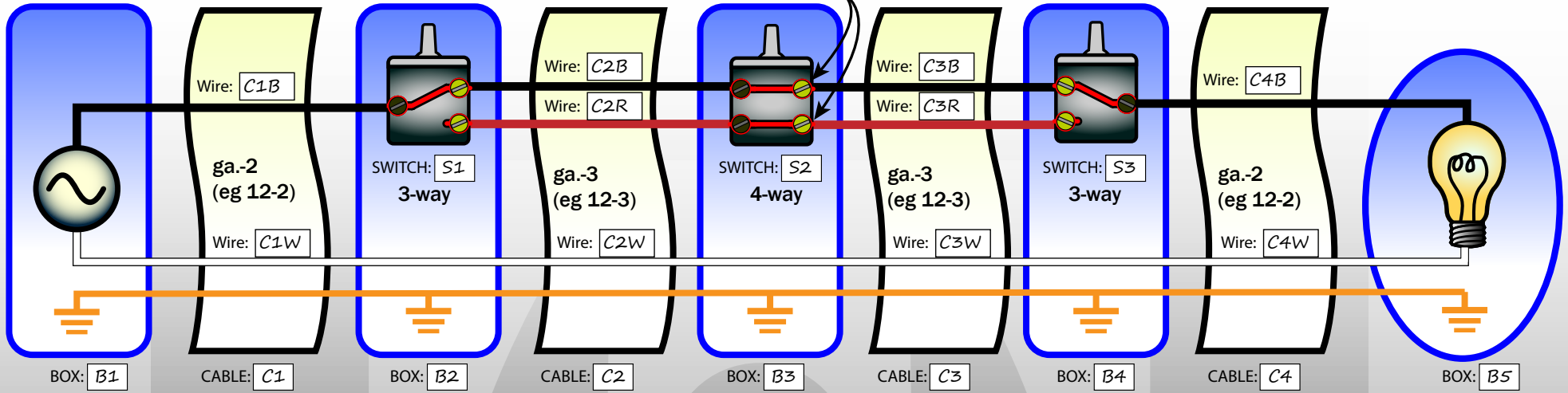


Example

Note: Travelling pairs can be swapped on like-colored terminals of any switch



Note: In existing installations neutrals may not be present within each box. You may need to draw addition boxes or even the same box between multiple switches to clearly show the circuit yet depict all cables.

